

# ECE 1895 - ASSIGNMENT 5 REPORT

Yinhao Qian

September 9, 2022

## 1 SPICE Verification


There are going to be two versions of the spice simulation: one is for the actual PCB design and one is solely for testing purpose only. The reason I would have to create a separate ones for testing and PCB design is **I was unable to find capacitors with large values (more than 1  $\mu\text{F}$ ) in Benedum 1223**, so I have decided to replace all capacitors with values more than 1 $\mu\text{F}$  with 1 $\mu\text{F}$ . If everything goes well, the only changes should be the frequency of oscillations and nothing else. I'll demonstrate this is the case in the upcoming sections.

### 1.1 Version 1 - SPICE for PCB Design


For resistor designated with  $R909$  and  $R501$ , I would simplify the circuit by combining them into a new resistor designated with  $R909R501$ , and I'll change simulate the circuit two times with each resistances.

### 1.1.1 Schematics

**This is when 511 Ohm is used:**

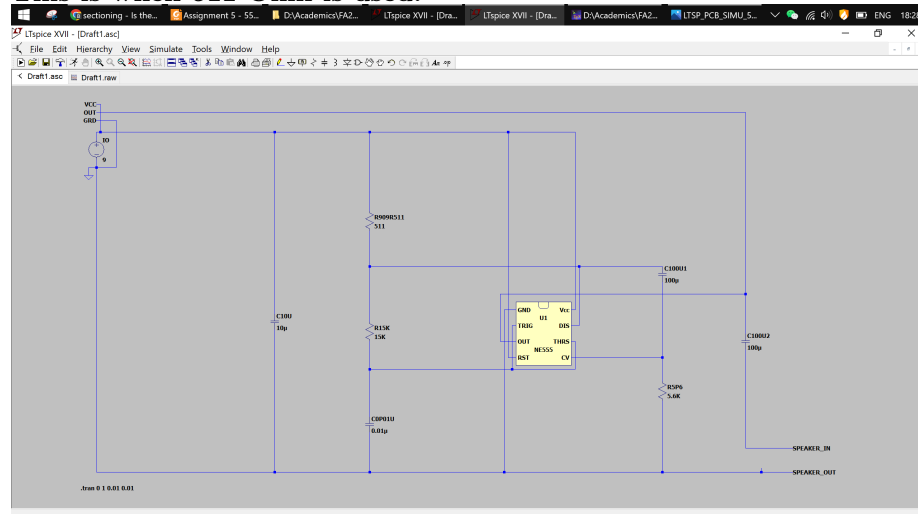

This is when 909 Ohm is used:

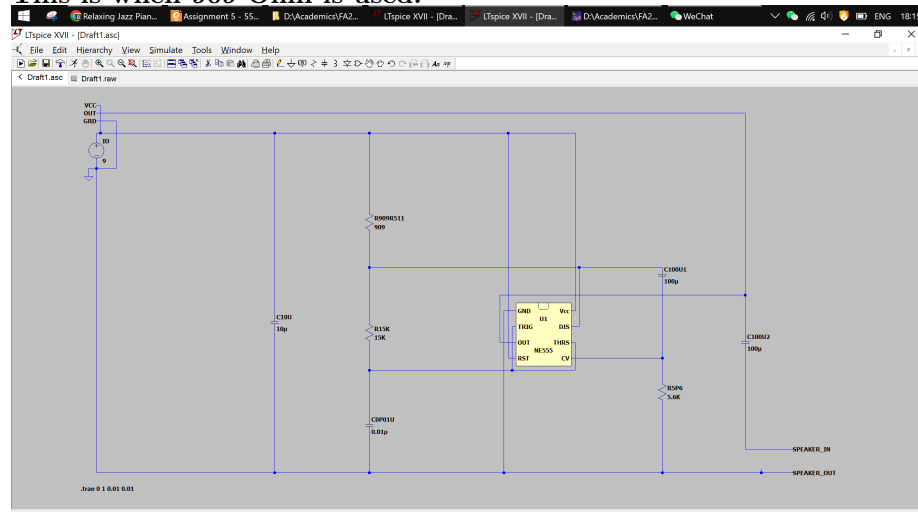


No other changes are made except for the resistor values.

### 1.1.2 Simulation

This is when 511 Ohm is used:



This is when 909 Ohm is used:

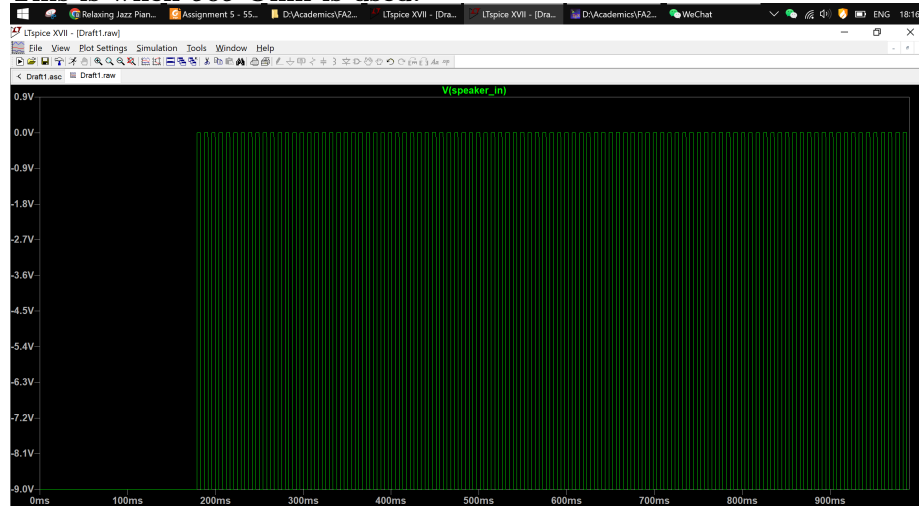


An interesting observation here is that the resistance of  $R_{909R511}$  is **directly proportional** to the frequency of generated output.

## 1.2 Version 2 - SPICE for Breadboard Testing


For resistor designated with  $R_{909}$  and  $R_{501}$ , I would simplify the circuit by combining them into a new resistor designated with  $R_{909R501}$ , and I'll generalize the model by using a 1K-Ohm resistor, since it's the one I found in Benedum 1223.
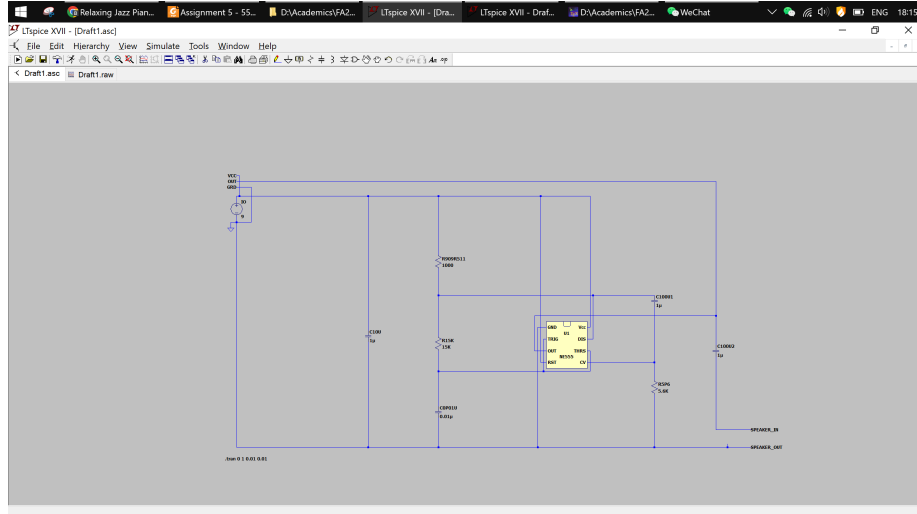
### 1.2.1 Schematics

Note that all capacitors with capacitance greater than  $1\mu F$  are replaced with capacitors of  $1\mu F$ .




### 1.2.2 Simulation

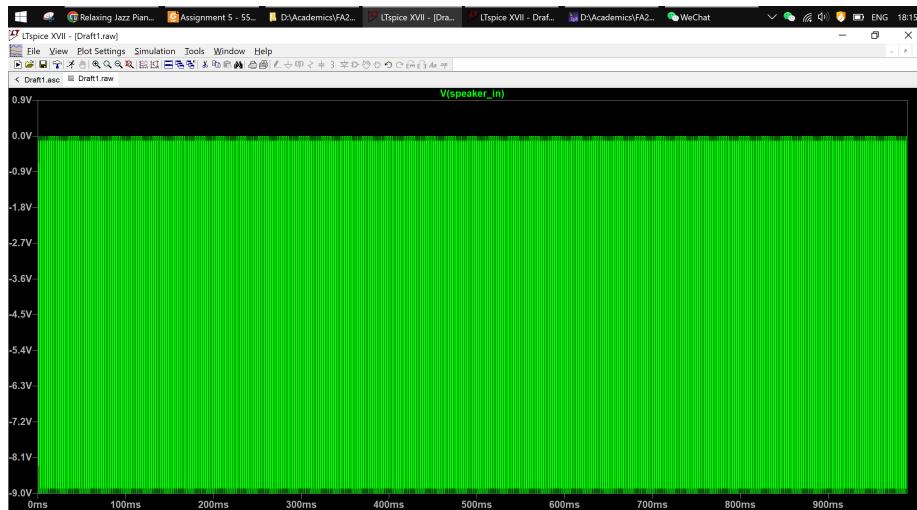

We have noticed that the frequency does increased a lot, but as long as our measured voltage oscillates, we are good to go.
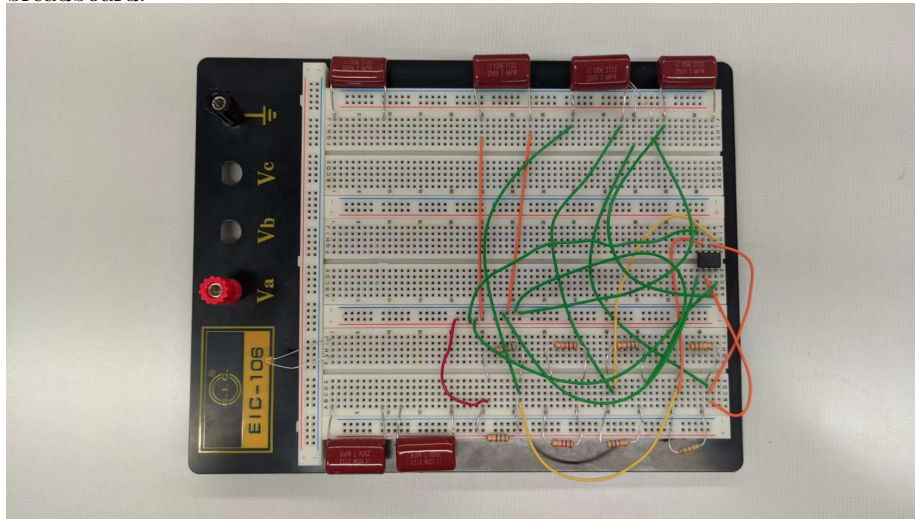
## 2 Breadboard Verification

I have connected wires and attempted to make matching circuits with reference to the schematics we made from previous section. Here's what it looks like on breadboard:



I understand it looks messy, that's why I hereby provide an visual aid with column/row numbers and wire-coloring matches.

