

Junior Design


555 Timer Design Improvements

Samuel Dickerson, Ph.D.
ECE Department
University of Pittsburgh




555 Timer Reflection

Hans Camenzind

 

 Any final comments on why the 555 design has been so resilient for so long?




555 Timer Lessons



- A “perfect” design is not possible
- A “perfect” design is also not always necessary
- Always room for improvements and design iterations

Is there anything you would like to redo with your 555 timer design?



555 Timer Design Reflection

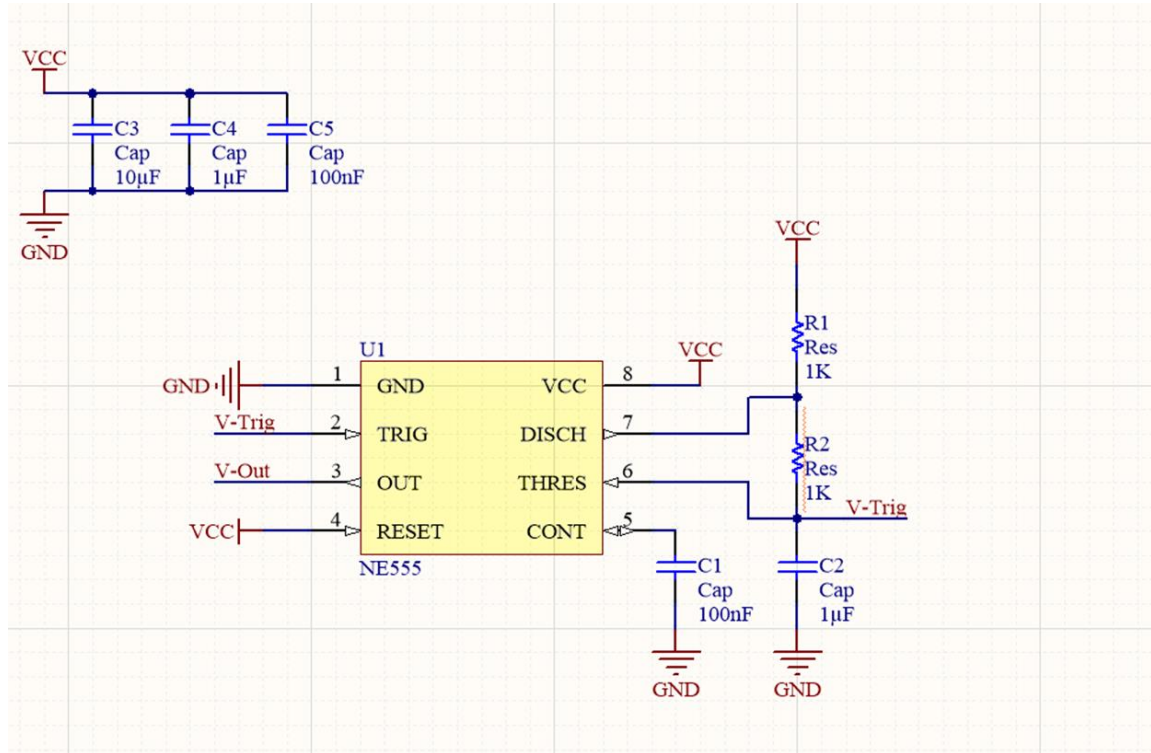

Decoupling Capacitors

  


Decoupling Capacitors

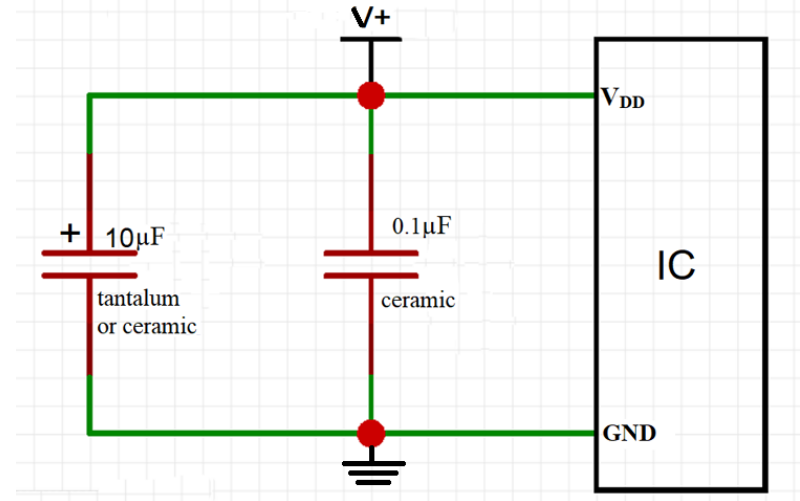 

- Large capacitor placed away from IC to smooth out low frequency changes
- Small capacitors placed closer to the IC to smooth high frequency changes

Design Reviews

 


In the IEEE Article, you mentioned that there was a design review at Signetics. Was that a contractual obligation?


No. I just thought it was a good idea. I've always had design reviews for all my designs. Get feedback, bounce off ideas with colleagues. But, just how laborious the design was. First, the breadboarding of the circuit. The one thing you want to do is make sure the circuit works well in production, and in production you have parameter variation - high gain, low gain for transistors, high resistor values, low resistor values, all sorts of combinations.

The diagram shows a circuit layout on a grid. On the left, a transformer P1 is connected to a series of capacitors C3, C4, and C5. These capacitors are connected to the input of an NE555 timer U1. The timer U1 is connected to a network of resistors R1, R2 and capacitors C1, C2. The output of the timer is connected to a load. The circuit is dimensioned with a width of 3000.00 and a height of 3000.00.


555 Timer Design Review

 


Vs.

 


555 Timer Design Review

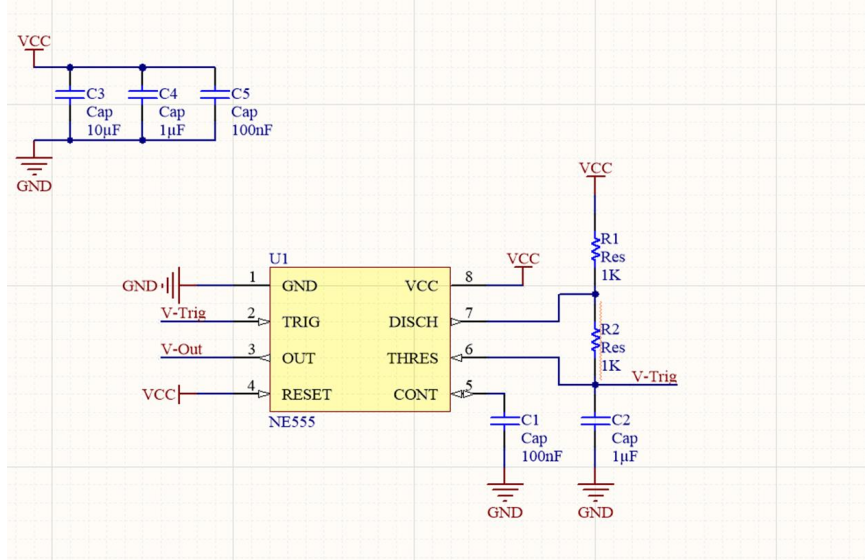

How can we make this design better?

 

Trace Impedance

 


x = length of trace (cm)
 w = width of trace (cm)
 h = height of trace (cm)
 t = thickness of trace (cm)
 ϵ_r = PCB Permeability

$$Z_0(\Omega) = 31.6 \sqrt{\frac{L(nH)}{C(pF)}}$$

$$L(nH) \approx 2x \ln\left(\frac{5.98 h}{0.8 w + t}\right)$$


$$C(pF) \approx \frac{0.264x (\epsilon_r + 1.41)}{\ln\left(\frac{5.98 h}{0.8 w + t}\right)}$$

$$T_p (ps/cm) = 31.6 \sqrt{L(nH)C(pF)}$$

 

$$C(pF) \approx \frac{0.0886 \epsilon_r A}{h}$$

 h = separation between planes (cm)
 A = area of common planes = $l \cdot w$ (cm²)
 ϵ_r = PCB Permeability



$$L(nH) \approx \frac{h}{5} \left[1 + \ln\left(\frac{4h}{d}\right) \right]$$


$$C(pF) \approx \frac{0.0555 \epsilon_r h d_1}{d_2 - d_1}$$

$$Z_0(\Omega) = 31.6 \sqrt{\frac{L(nH)}{C(pF)}}$$

$$T_p (ps/cm) = 31.6 \sqrt{L(nH)C(pF)}$$

- Every trace, plane, and via has an associated inductance, capacitance, and resistance
- Impact on PCB depends on both frequency and dimensions

Ground Planes

 


Light green area is the “ground plane”

PCB's often contain “Ground Planes”


- Makes layout easier
- Ensures ground is consistent
- Reduces elective noise / crosstalk and ground loops

Can we make the design better?


555 Timer Design Review

 



Vs.

 


Vs.

 

555 Timer Design Review

 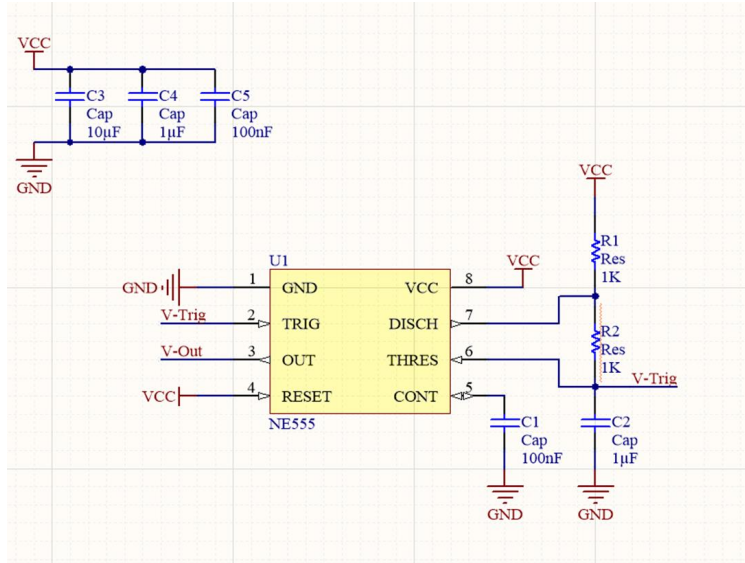

Surface Mount Components

 

\$0.45



\$0.36



Current Tasks

- 1. Review your project proposal**
- 2. Prepare Bill of materials for your design project (Digikey)**
- 3. Start Constructing Schematic**
- 4. Verify your design**